


Q1 Using Multisim online simulator to design a CMOS NOR Gate, verify the truth table and show timing diagram wave form.



PMOS

NMOS

A	B	Q ₁	Q ₂
0	0	0	0
0	1	0	1
1	0	1	0
1	1	1	1

Q ₃	Q ₄	Count
0	0	1
0	1	0
1	0	0
1	1	0

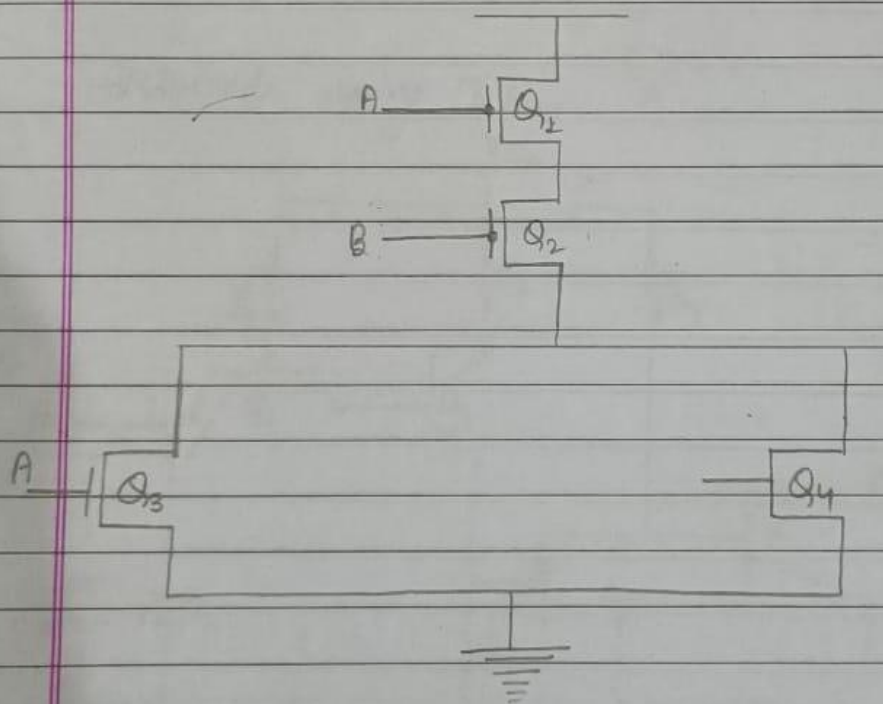

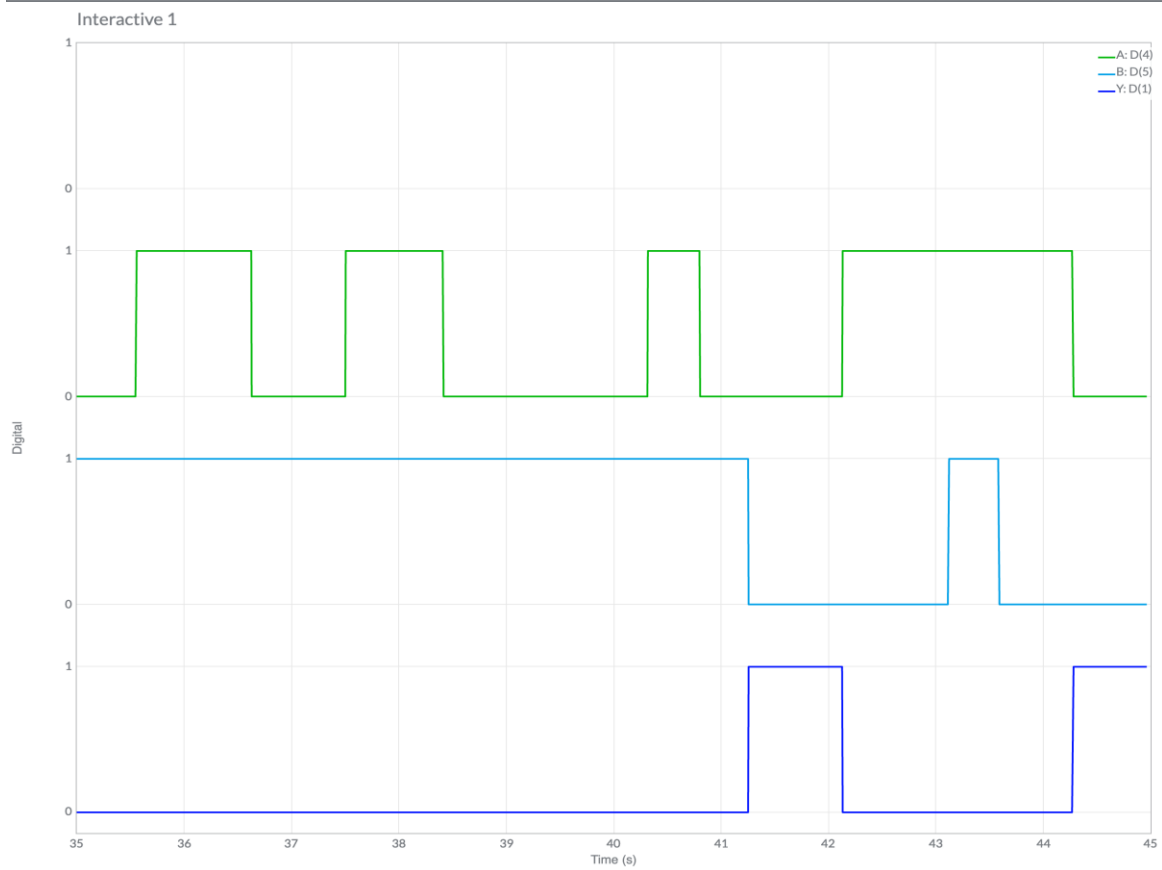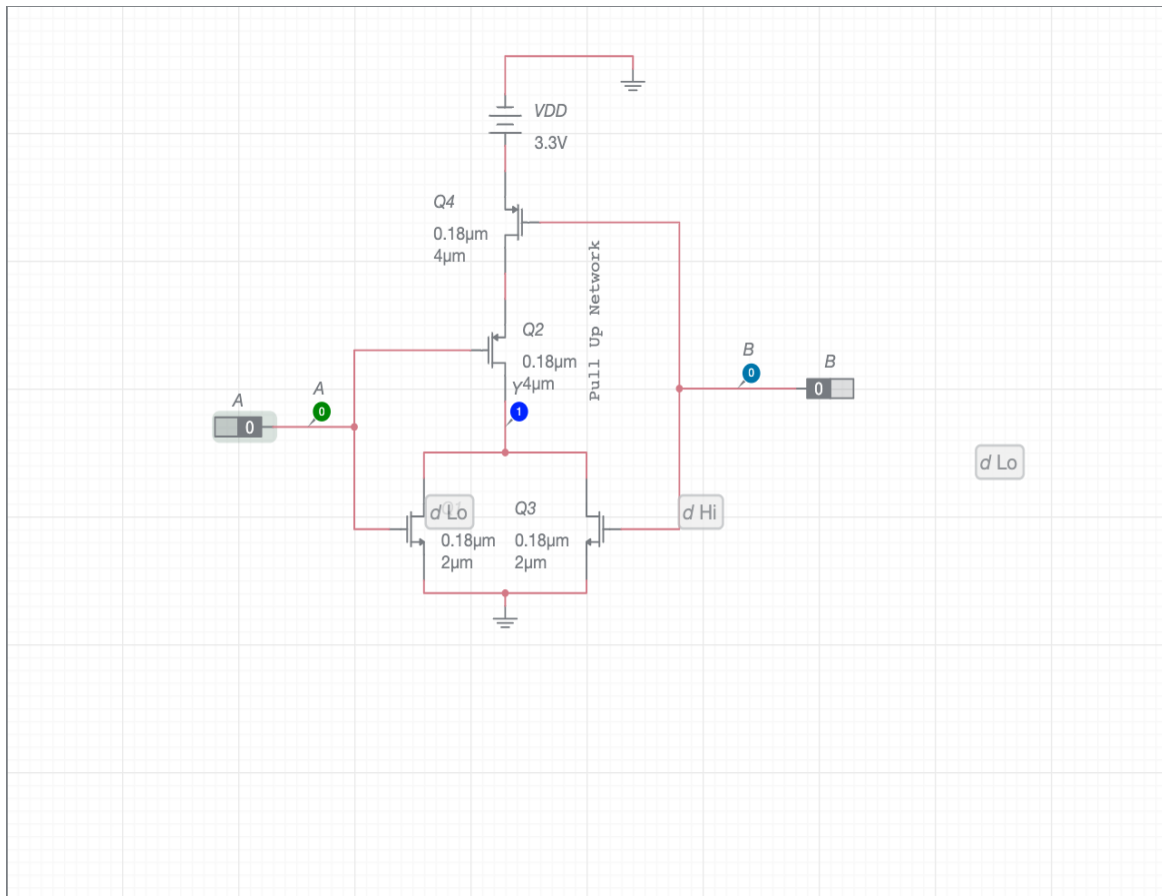

Q3 Find the minimal sum of products for the Boolean expression, $f(w, x, y, z) = \sum(1, 3, 4, 5, 9, 10, 11) + \sum p(6, 8)$ using the Quine-McCluskey Method.


1	0	0	0	1	1	0	0	0	1	(1,3)	0	0	-	1
3	0	0	1	1	4	0	1	0	0	(1,5)	0	-	0	1
4	0	1	0	0	8	1	0	0	0	(1,4)	-	0	0	1
5	0	1	0	1	3	0	0	1	1	(4,5)	0	1	0	-
6	0	1	1	0	5	0	1	0	1	(4,6)	0	1	-	0
8	1	0	0	0	6	0	1	1	0	(8,9)	1	0	0	-
9	1	0	0	1	9	1	0	0	1	(8,10)	1	0	-	0
10	1	0	1	0	10	1	0	1	0	(8,11)	-	0	1	1
11	1	0	1	1	11	1	0	1	1	(9,11)	1	0	-	1
										(10,11)	1	0	1	-

(1, 9, 3, 11) - 0 - 1

(8, 9, 10, 11) 1 0 - -

(8, 10, 9, 11) 1 0 - -

Left Minterm

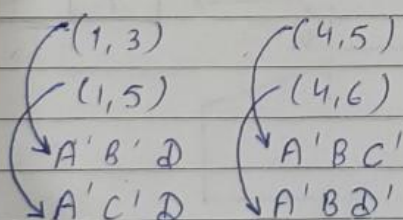

Matched:

$(1, 9, 3, 11)$ $(8, 9, 10, 11)$
 $B'D$ AB'

Final Table

			1	3	4	5	9	10	11
A'	B'	D	X	X					
A'	C'	D	X			X			
A'	B	C'			X	X			
A'	B	D'			X				
B'	D		X	X					
A	B'					X		X	
B'	D					X	(X)	X	
A	B'								

$$Y = AB'$$

- Q4 Create the logic diagram and logic symbol of IC 74154 4 to 16 decoder and briefly explain its functions.
- The IC 74154 is a 4 to 16 decoder. It decodes four binary weighted address inputs to 16 mutually exclusive outputs. The device features two input pins.
- A high on either of the input enables the output high. The device can be used as 1 to 16 demultiplexer by using one of the enabled inputs as the multiplied data input. When the other enabled input is low, the addressed output will follow the state of the applied data.